

**RADIO ENGINEERING I
HOME ASSIGNMENT 4/2025 HW4**

Return by 28.11.2025 @20.00

Return your answer into Moodle.**Write tag HW4, your name, and student ID on
all sheets you are returning.**

Name _____

Student ID _____

A transistor has the following S parameters at 2.8 GHz:

$$S_{11} = 0.49 \angle -103^\circ$$

$$S_{12} = 0.0 \angle 0^\circ$$

$$S_{21} = 3.4 \angle 53^\circ$$

$$S_{22} = 0.65 \angle -72^\circ$$

Design an amplifier that has the maximum gain. What is the maximum transducer power gain? Use lossless lumped components when designing the matching for the input and the output. Load and source impedance are 50Ω .