



FACULTY OF INFORMATION TECHNOLOGY AND ELECTRICAL ENGINEERING

DEGREE PROGRAMME IN ELECTRONICS (MASTER'S)

Course Name: Radio Engineering 1

Homework #5

Name: Arafat Miah

Student No: 2512200

Fall 2025

Aravind Mah.
ID: 2512200

Solⁿ.

(a). We can determine the stability of the transistor by using Δ , K parameters which is defined below with μ .

i). $|\Delta| < 1$.

ii). $K > 1$

iii). $\mu > 1$.

Here, $|\Delta| = |S_{11}S_{22} - S_{12}S_{21}|$
 $= (0.70 \angle -155)(0.66 \angle -55) - (0.07 \angle 32)(3.0 \angle 77)$
 $= -0.33 + j0.03$
 $= 0.33 \angle 174.4$

$|\Delta| < 1$, valid

Now,
 $K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{12}S_{21}|}$
 $= \frac{1 - 0.70^2 - 0.66^2 + 0.33^2}{2 \cdot 0.211}$
 $= 0.4364$

$K < 1$ not valid

As we can see that $K < 1$, Unconditionally stable is not true for the transistor. So, the instability depends on matching of the input and output. i.e. So, it can become unstable for certain passive source or load impedance. From Pozar it is stated that, "If a two port network is unconditionally stable, it will not oscillate for any passive source and load impedance."

⑤ Input stability circle:-

$$\text{Center, } c_s = \frac{(s_{11} - a s_{22}^*)^*}{|s_{11}|^2 - |a|^2} = \frac{0.70 \angle 155 - [(0.33 \angle 174.4)(0.66 \angle 55)]^*}{0.70^2 - 0.33^2}$$

$$= \frac{0.5 \angle +165.45}{0.380}$$

$$= 1.34 \angle +165.45$$

$$\text{Radius, } R_s = \left| \frac{s_{12} s_{21}}{|s_{11}|^2 - |a|^2} \right| = \frac{(0.7 \angle 32)(3 \angle 77)}{0.7^2 - 0.33^2}$$

$$= -0.179 + j0.52$$

$$= 0.55$$

$$\therefore R_s = 0.55$$

$$c_s = 1.34 \angle +165$$

Output Circle:-

$$c_L = \frac{(s_{22} - a s_{11}^*)}{|s_{22}|^2 - |a|^2} = \frac{0.66 \angle 55 - (0.33 \angle 174)(0.70 \angle 155)}{0.66^2 - 0.33^2}$$

$$= 1.3 \angle 67.3$$

So

$$R_L = \left| \frac{s_{12} s_{21}}{|s_{22}|^2 - |a|^2} \right| = \frac{(0.07 \angle 32)(3 \angle 77)}{0.66^2 - 0.33^2}$$

$$= 0.64 \angle 100$$

∴

So

$$\boxed{R_L = 0.64}$$

$$\boxed{c_L = 1.3 \angle 67.3}$$



(c) $Z_L = 5 + 7.5j$

$\therefore Z_L = \frac{5 + 7.5j}{50} = 0.1 + 1.5j$ (Normalized)

Reflection, $\Gamma_L = \frac{Z_L - 1}{Z_L + 1} = \frac{0.1 + 1.5j - 1}{0.1 + 1.5j + 1}$
 $= 0.94 \angle 67.2^\circ$

Now, the input reflection co-efficient of the transistor is,

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$= 0.70 \angle -15.5^\circ + \frac{0.2 \angle 77.5^\circ}{1 - 0.6 \angle 12.5^\circ}$$

$$= -1.08 - j0.4065$$

$$\therefore |\Gamma_{in}| = \sqrt{1.08^2 + (0.4065)^2} = 1.15 > 1$$

Here,

$$S_{12} S_{21} \Gamma_L = 0.21 \angle 109^\circ \times 0.94 \angle 67.2^\circ$$

$$= 0.2 \angle 176.5^\circ$$

$$S_{22} \Gamma_L = 0.66 \angle -5.7^\circ \times 0.94 \angle 67.2^\circ$$

$$= 0.6 \angle 12.5^\circ$$


So, using part b, we determined that the stable region is situated outside the stability circle. For the given load, reflection co-efficient falls inside the circle, which places the device in an unstable region. In this condition, the magnitude of the input reflection co-efficient becomes ^{larger} than one meaning that the reflected wave is greater than the incident wave in input.

NAME <i>Arabat Mian</i>	TITLE <i>Radio Engineering I.</i>	DWG. NO. <i>01</i>
SMITH CHART FORM ZY-01-N		DATE
Microwave Circuit Design - EE523 - Fall 1999		

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

output.

Input

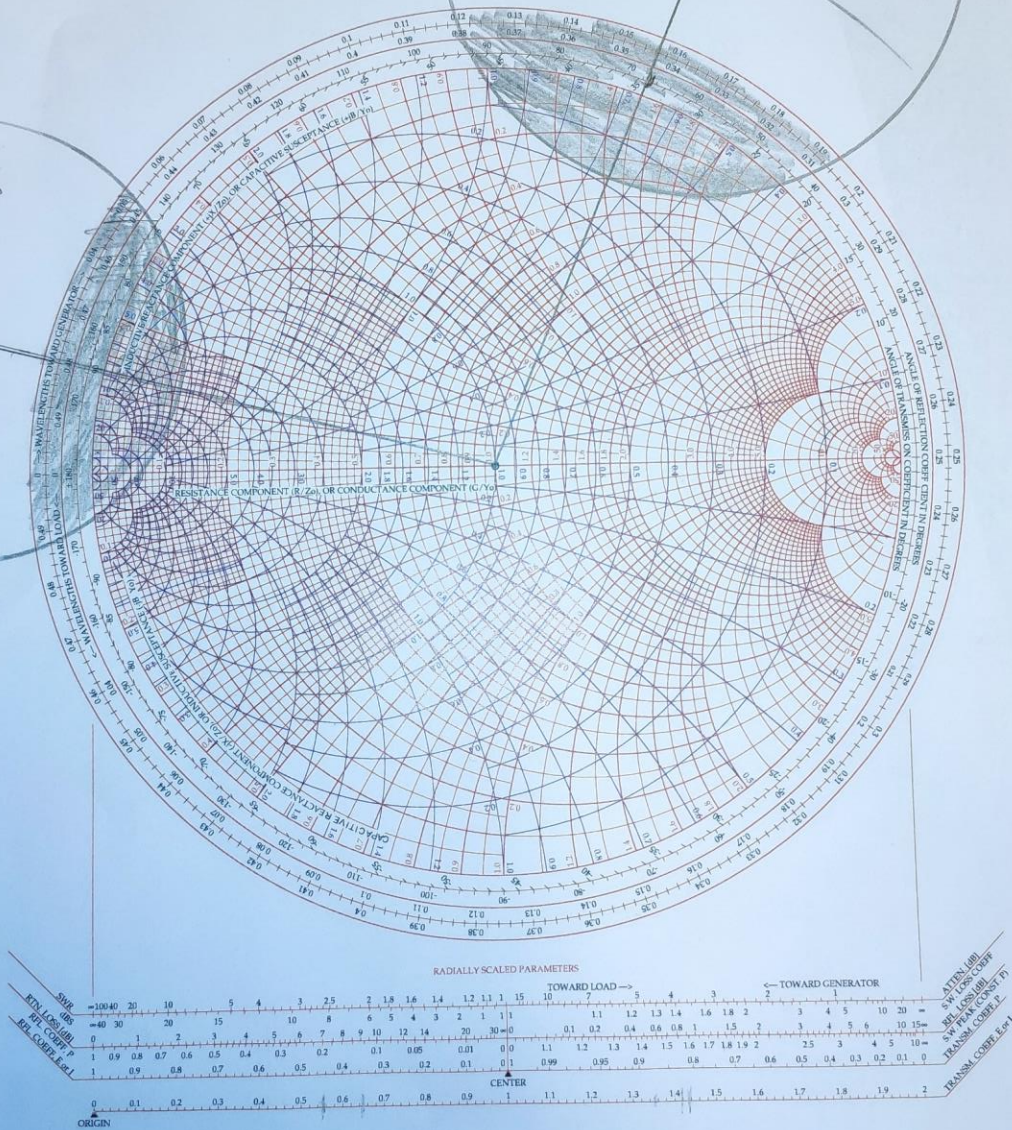

SHOT ON MI 9T
AI TRIPLE CAMERA