

RADIO ENGINEERING I
HOME ASSIGNMENT 1/2025 HW1

Return by 7.11.2025 @20.00

Return your answer into Moodle.**Write tag HW1, your name, and student ID on all sheets you are returning.**

Name _____

Student ID _____

- a) A transmitter is connected with a $50\ \Omega$ coaxial cable to an antenna ($Z_{in} = 80 - j40\ \Omega$). If the transmitter ($Z_{out} = 50\ \Omega$) can deliver 30 W when connected to a $50\ \Omega$ load, how much power is connected to the antenna?
- b) Design a lumped element L-section matching network to match a series RL load (with $R = 100\ \Omega$ and $L = 2.5\ \text{nH}$) to a $50\ \Omega$ line at 3.5 GHz. Don't use Smith chart when defining the required inductance and capacitance values. Show all equations and calculations in your answer.