

RADIO ENGINEERING I
HOME ASSIGNMENT 5/2025 HW3

Return by 5.12.2025 @20.00

Return your answer into Moodle.**Write tag HW5, your name, and student ID on all sheets you are returning.**

Name _____

Student ID _____

1.

The S-parameters of a transistor at a frequency of 3.4 GHz are

$$S_{11} = 0,70 \angle -155^\circ$$

$$S_{21} = 3,0 \angle 77^\circ$$

$$S_{12} = 0,07 \angle 32^\circ$$

$$S_{22} = 0,66 \angle -55^\circ$$

- Study the stability of the transistor. What does it mean if the transistor is unconditional stable?
- Define the stability circles for the input and the output. Furthermore, draw the stability circles on the Smith chart and define the stable regions.
- The unmatched transistor above is used to drive a load that is $Z_L = 5 + 75j$ Ohms . What may happen and why?