



FACULTY OF INFORMATION TECHNOLOGY AND ELECTRICAL ENGINEERING

DEGREE PROGRAMME IN ELECTRONIC'S (MASTER'S)

# **Course Name: Radio Engineering 1**

## **Homework #2**

Name: Arafat Miah

Student No: 2512200

Fall 2025

Home wor-2  
Arafat Miah  
2512200


Q1:  $Z_L = 140 - 75j \Omega$   
 $Z_0 = 50 \Omega$   
 $f = 2.45 \text{ GHz}$

So, Normalized value,

$$Z_L' = \frac{Z_L}{Z_0} = 2.8 - j1.5$$

Since,  $R_L > Z_0$ .

So,

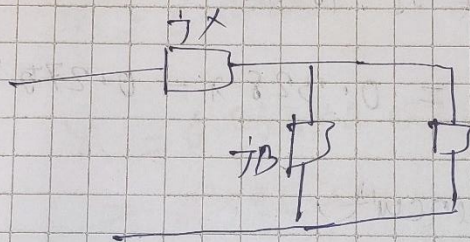

Now, we move from point A to point B on the admittance to add capacitance.

$$jB = j(0.48 - 0.16) = 0.32j$$


In order to add inductor in series of load, then we need to move from point B to the corner of the circle.

$$jX = 1.60j$$

Now, calculating the components,

$$C = \frac{B}{2\pi f Z_0} = \frac{0.32}{2\pi \times 2.45 \times 10^9 \times 50} = 0.415 \text{ pF}$$
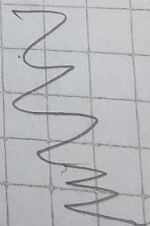
$$L = \frac{X}{2\pi f} = \frac{50 \times 1.60}{2\pi \times 2.45 \times 10^9} = 5.10 \text{ nH}$$





②. With the help of point A we draw USPW circle.

→ To find the intersect with  $1+jx$  circle (point B), then travel clockwise on the USPW circle.

Now, To compensate imaginary part of point B, we find point on USPW circle which is mirrored on the origin for point B. (Point C).

Now, the length of minor arc line for  $d_1$  is:-  
this will be the circumference from point A to point B.

$$\therefore d_1 = 0.328\lambda - 0.275\lambda = 0.053\lambda$$


For open circuit,

$$d_2 = 0.25 + 0.078\lambda$$

$$= 0.328\lambda$$

For short ckt,

$$d_3 = 0.078\lambda$$

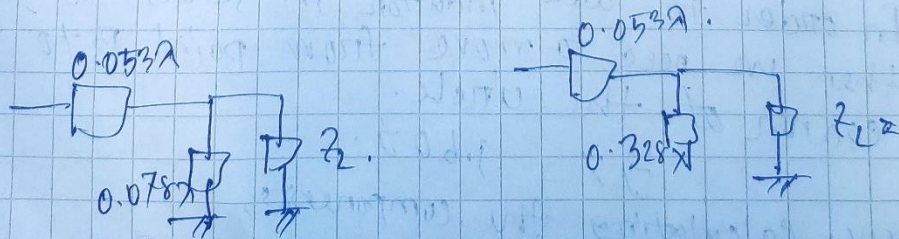



© Lumped & microstrip's component :-

Here, we can keep the value of shunt capacitance from part (a), we calculated.

Here, Imaginary part of admittance in point is compensated by connecting stub in series. So, we move from  $z_0$  clockwise to match of point B  $[E = -B]$  for compensation and find length of microstrip required :-

$[z_0 \text{ to point E}]$

Short circuit :  $Y = 0.072\lambda$


Open circuit :  $Y = 0.25\lambda + 0.072\lambda$   
 $= 0.322\lambda$

$[z_0 \text{ to point E}]$



NAME <u>Artafat Miah</u>	TITLE <u>Radio Engineering I</u>	DWG. NO. <u>01</u>
SMITH CHART FORM ZY-01-N		DATE
Microwave Circuit Design - EE523 - Fall 1999		

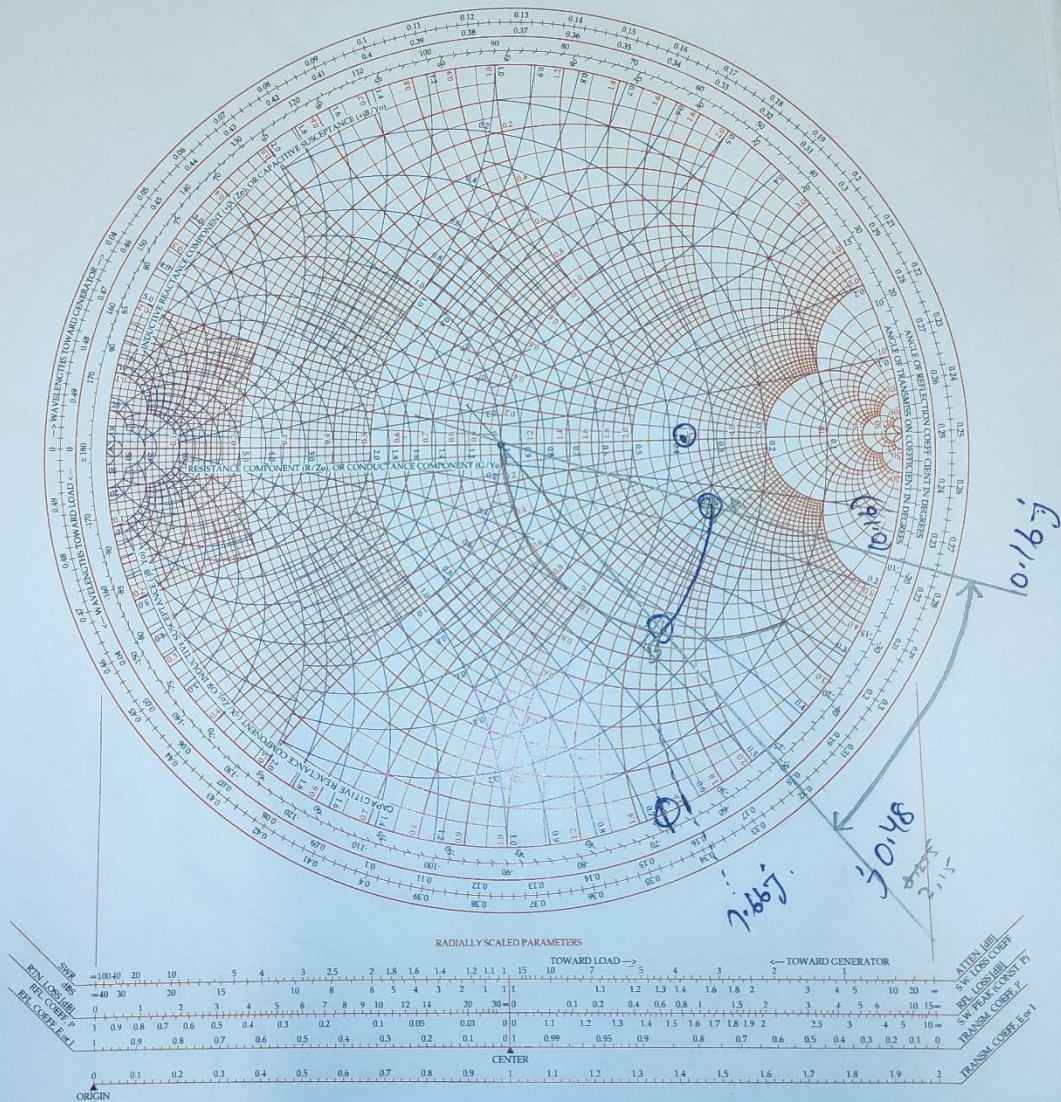
# NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES





NAME <u>Arabat Muan</u>	TITLE <u>Radio Engineering I.</u>	DWG. NO <u>02</u>
SMITH CHART FORM ZY-01-N		DATE
Microwave Circuit Design - EE523 - Fall 1999		

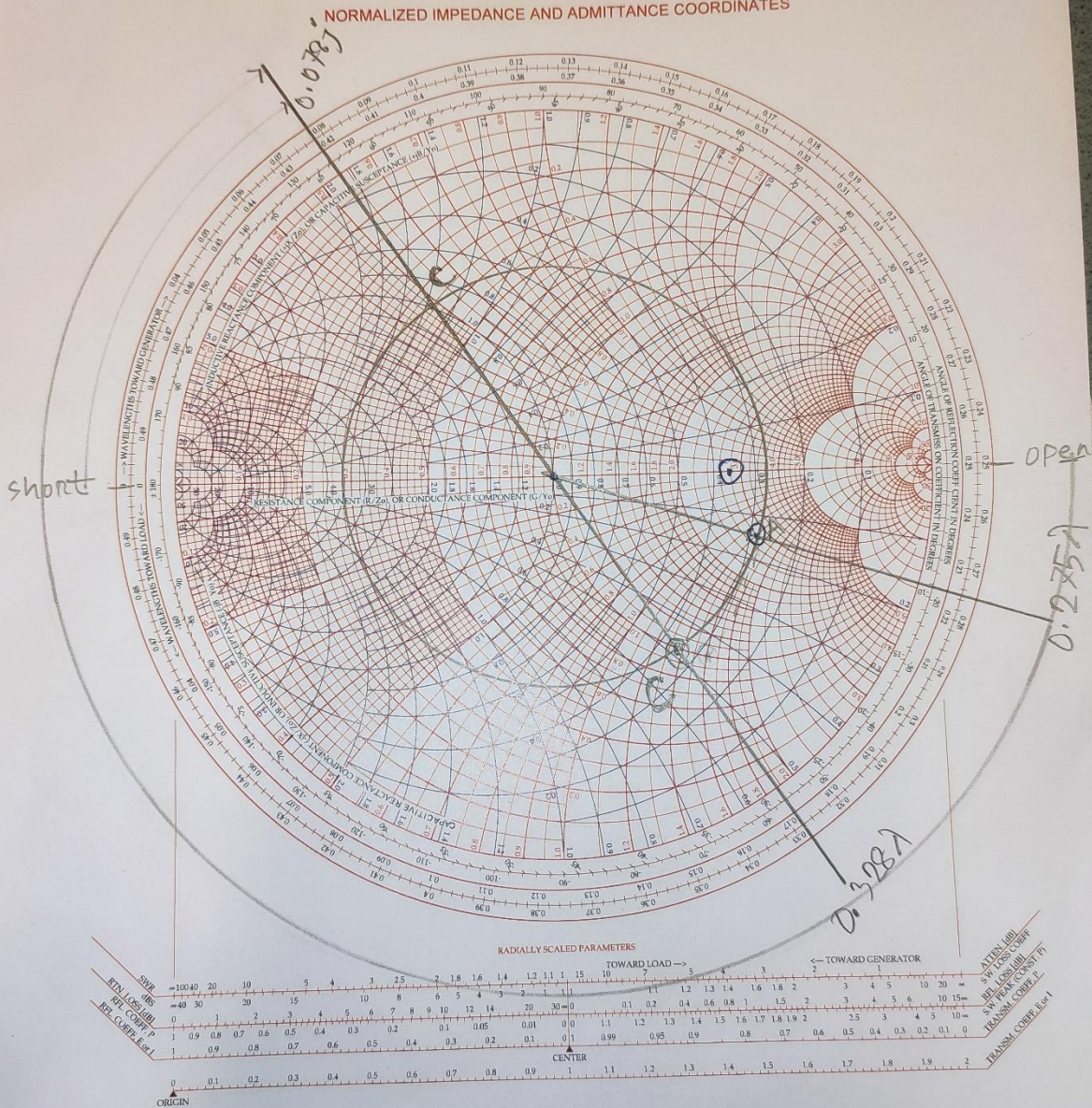NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



SHOT ON MI 9T  
AI TRIPLE CAMERA



NAME <i>Ararat Miah</i>	TITLE <i>Radio Engineering I</i>	DWG. NO. <i>03</i>
SMITH CHART FORM ZY-01-N		DATE
Microwave Circuit Design - EE523 - Fall 1999		

# NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

