



FACULTY OF INFORMATION TECHNOLOGY AND ELECTRICAL ENGINEERING

DEGREE PROGRAMME IN ELECTRONICS (MASTER'S)

Course Name: Radio Engineering 1

Homework #06

Name: Arafat Miah

Student No: 2512200

Supervisor: **Aarno Pärssinen &** Kimmo Rasilainen

Fall 2025

Arafat Mah

ID: 2512200.

Question:- Design a Portion of an RF receiver with Bandpass filter, low noise Amplifier and mixer.

Filter: Insertion loss = -1.5 dB .

LNA: $G = 12 \text{ dB}$, $NP = 2.5 \text{ dB}$.

Mixer M: $G = 5 \text{ dB}$, $NP = 8 \text{ dB}$.

Task ① \Rightarrow In what order should these components be placed to achieve the lowest NP in the system.

\Rightarrow First, we need to place the lowest noise figure and high gain, this will help us to reduce the overall system noise figure. Also that the noise contributions of subsequent stages are divided by the gain. Finally, the overall noise gets attenuated.

Now, using the Friis Formula:-

Converting gain & NP to linear unit:-

$$G_F = 10^{-1.5/10} = 0.708$$

$$F_{BP} = 10^{1.5/10} = 1.413$$

$$G_A = 10^{12/10} = 15.849$$

$$F_A = 10^{2.5/10} = 1.778$$

$$G_M = 10^{5/10} = 3.162$$

$$F_M = 10^{8/10} = 6.3$$

We have three components, ^{we} so we can cascade the in $(2^3 - 2) = 6$ ways.

The Friis formula with G_1, G_2, G_3 and F_1, F_2, F_3 cascaded is,

$$F_{\text{total}} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2}$$



ORDER	F _{noise}	F _{total}	10 log F.
F → A → M	$1.413 + \frac{1.778-1}{0.708} + \frac{6.3-1}{0.708 \times 15.849}$	2.084	4.748
F → M → A	$1.413 + \frac{6.3-1}{0.708} + \frac{1.778-1}{0.708 \times 3.162}$	0.246	0.659
A → F → M	$1.778 + \frac{1.4-1}{15.849} + \frac{6.3-1}{15.849 \times 0.708}$	2.277	3.57
A → M → F	$1.778 + \frac{6.3-1}{15.849} + \frac{1.413-1}{15.849 \times 3.162}$	2.12	3.264
M → F → A	$6.3 + \frac{1.413-1}{3.162} + \frac{1.778-1}{3.162 \times 0.708}$	6.778	8.31
M → A → F	$6.3 + \frac{1.778-1}{3.162} + \frac{1.413-1}{3.162 \times 15.849}$	6.55	8.165

Here, the connection which has the LNA first with the mixer and last the filter provides the minimum noise figure for the system.



Maximum Gain :-


It is the product of all the stages gain and it does not depend on any kind of ordering :-

So,

$$G_{\text{total}} = -1.5 + 12 + 15 = 15.5 \text{ dB.}$$

Conclusion :-

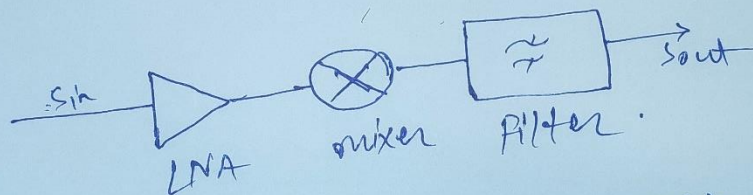So, the least noise figure for the RF receiver chain is :-



The NF of this system is 3.264
Overall system gain is 15.5 dB.